

**Rajshahi University of Engineering and
Technology**
Course Title: Sessional Based on CSE 2203
Course Code: CSE 2204
Lab Report - 07

Submitted to
Dr. Boshir Ahmed
Professor,
Computer Science and Engineering, RUET

Md. Zahirul Islam
Lecturer,
Computer Science and Engineering, RUET

Submitted by
Mrityika Roy
Roll: 1803175
Section: C
Computer Science and Engineering, RUET

Date of Submission: 07.08.2021

8.1

1. Name of the Experiment:

Verify SR Flip-Flop by using Module.

2. Objectives:

- To know the SR flip flop and its output
- To verify the outputs using module

3. Theory:

In a SR flip-flop module in Logisim, when the clock triggers, the value remembered by the flip-flop remains unchanged if R and S are both 0, becomes 0 if the R input (*Reset*) is 1, and becomes 1 if the S input (*Set*) is 1. If both inputs are 1, the value in the flip flop remains unchanged in logisim. But usually this case produces invalis condition in the flip-flop.

4. Experimental Analysis:

i. Circuit:

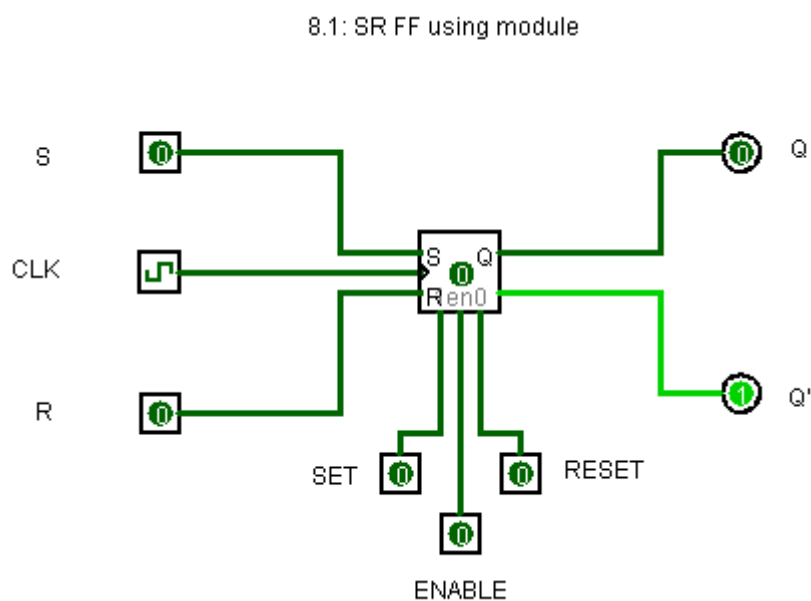


Figure: SR flip-flop using module

ii. Truth Table: For SR module

S	R	Q
0	0	Unchanged
0	1	0
1	0	1
1	1	Invalid(unchanged in Logisim)

5. Conclusion:

From the above experiment, it is verified that the output is the same as the implemented flip-flop using logic gates.

8.2

1. Name of the Experiment:

Verify JK Flip-Flop by using Module.

2. Objectives:

- To know the JK flip flop and its output
- To verify the outputs using module

3. Theory:

In a SR flip-flop module in Logisim, when the clock triggers, the value remembered by the flip-flop toggles if the J and K inputs are both 1, remains the same if they are both 0; if they are different, then the value becomes 1 if the J (*Jump*) input is 1 and 0 if the K (*Kill*) input is 1.

4. Experimental Analysis:

i. Circuit:

8.2: JK FF using module

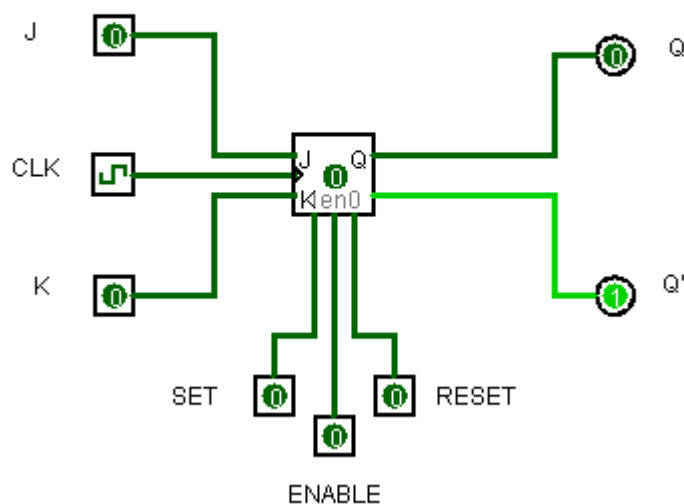


Figure: JK flip-flop using module

ii. Truth Table: For JK module

J	K	Q
0	0	Unchanged
0	1	0
1	0	1
1	1	Q'(Toggle)

5. Conclusion:

From the above experiment, it is verified that the output is the same as the implemented flip-flop using logic gates.

8.3

1. Name of the Experiment:

Verify D Flip-Flop by using Module.

2. Objectives:

- To know the D flip flop and its output
- To verify the outputs using module

3. Theory:

In a D flip-flop module in Logisim, when the clock triggers, the value remembered by the flip-flop becomes the value of the D input (*Data*) at that instant.

4. Experimental Analysis:

i. Circuit:

8.3: D FF using module

 


Figure: D flip-flop using module

ii. Truth Table: For D module

D	Q
0	0
1	1

5. Conclusion:

From the above experiment, it is verified that the output is the same as the implemented flip-flop using logic gates.

8.4

1. Name of the Experiment:

Verify D Flip-Flop by using Module.

2. Objectives:

- To know the D flip flop and its output
- To verify the outputs using module

3. Theory:

In a T flip-flop module in Logisim, when the clock triggers, the value remembered by the flip-flop either toggles or remains the same depending on whether the T input (*Toggle*) is 1 or 0.

4. Experimental Analysis:

i. Circuit:

8.4: T FF using module

 


Figure: T flip-flop using module

ii. Truth Table: For T module

T	Q
0	Q
1	Q'

5. Conclusion:

From the above experiment, it is verified that the output is the same as the implemented flip-flop using logic gates.