

**Rajshahi University of Engineering and  
Technology**  
**Course Title: Sessional Based on CSE 2203**  
**Course Code: CSE 2204**  
**Lab Report - 03**

**Submitted to**  
**Md. Zahirul Islam**  
**Lecturer,**  
**Computer Science and Engineering, RUET**

**Submitted by**  
**Mrityika Roy**  
**Roll: 1803175**  
**Section: C**  
**Computer Science and Engineering, RUET**

**Date: 20.03.2021**

## 4.1

### 1. Name of the Experiment:

Implementation of Various Logic Functions (For Example  $F(a, b, c, d) = \text{SOP}(0, 2, 3, 4, 6, 10, 14, 15)$ ).

### 2. Objectives:

- To know about SOP
- To know about minterms
- To know about the use of minterms
- To know the implementation of logic function using canonical form

### 3. Theory:

The full form of SOP is 'Sum of Products'. Boolean functions expressed as a sum of minterms or product of maxterms are said to be in canonical form. A Boolean function can be expressed, canonically, as a sum of minterms, where each minterm corresponds to a row (of the function's truth table) whose output value is 1.

## 4. Experimental Result Analysis:

### i. Circuit:

4.1.1: Implementation of Various Logic Function (For example:  $F(a,b,c,d) = \text{SOP}(0,2,3,4,6,10,14,15)$ ) using Drag and drop.

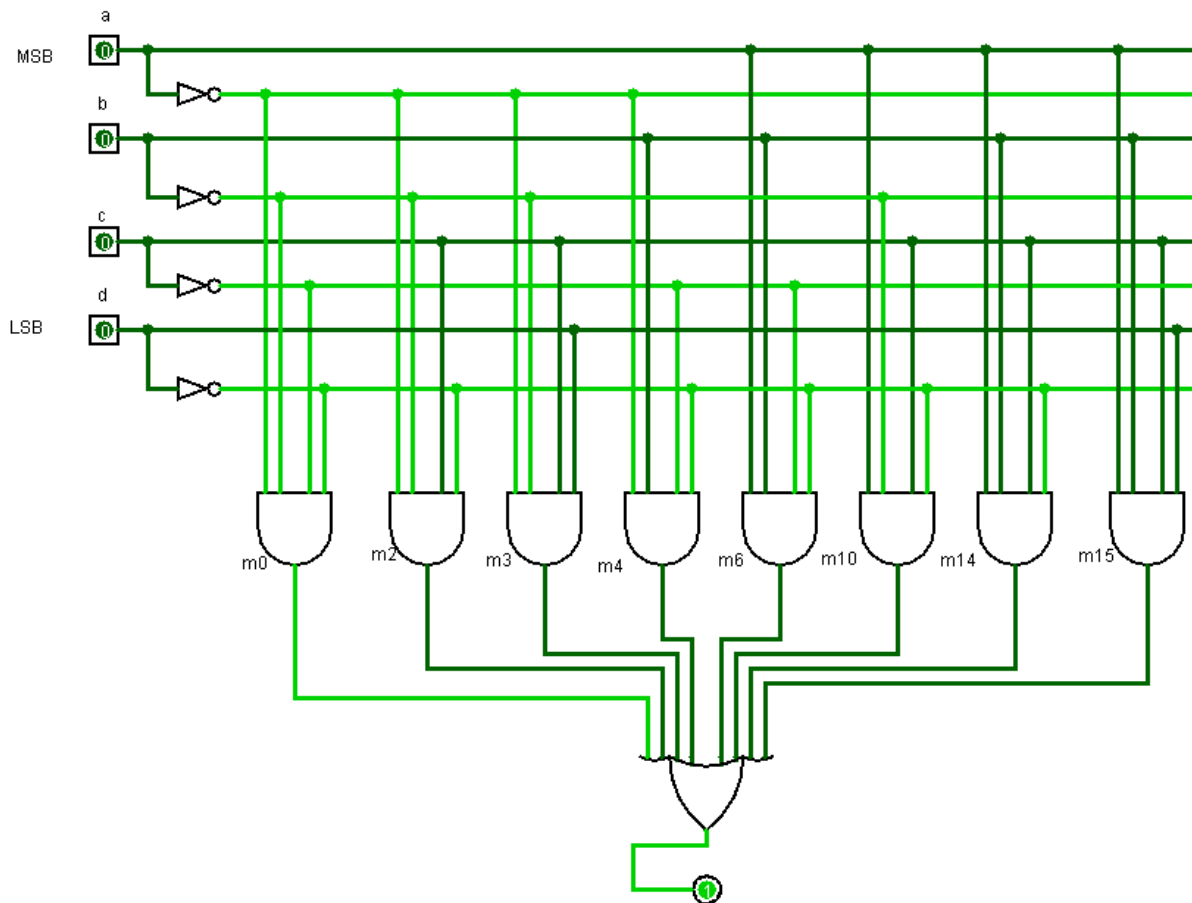


Figure: Circuit Diagram for the Given Function Using Drag and Drop

4.1.2 Implementation of Various Logic Function (For example:  $F(a,b,c,d) = \text{SOP}(0,2,3,4,6,10,14,15)$ ) Using Circuit Analysis

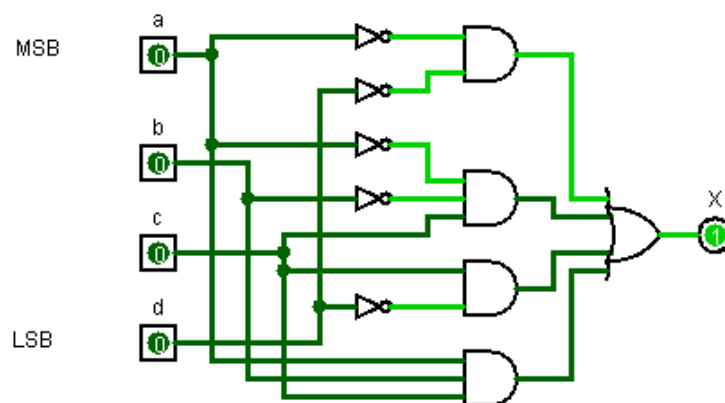


Figure: Circuit Diagram for the Given Function Using Circuit Analysis

## ii. Truth Table:

| a | b | c | d | x |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

## 5. Conclusion:

From the above experiment we can conclude that we can implement any logic function as the sum of minterms.

$$\begin{aligned}
 & \bar{a}\bar{b}\bar{c}\bar{d} + \bar{a}\bar{b}c\bar{d} + \bar{a}\bar{b}c d + \bar{a}b\bar{c}\bar{d} + \bar{a}b\bar{c}d + \bar{a}b c \bar{d} + \bar{a}b c d + abcd \\
 = & \bar{a}\bar{b}\bar{d} + \bar{a}\bar{b}c\bar{d} + \bar{a}\bar{b}c d + \bar{a}b\bar{c}\bar{d} + \bar{a}b\bar{c}d + \bar{a}b c \bar{d} + \bar{a}b c d + abcd \\
 = & \bar{a}\bar{d}(\bar{b} + b\bar{c}) + \bar{a}\bar{b}c\bar{d} + \bar{a}\bar{b}c d + \bar{a}b\bar{c}\bar{d} + \bar{a}b c \bar{d} + abcd \\
 = & \bar{a}\bar{d}(\bar{b} + c) + \bar{a}\bar{b}c\bar{d} + \bar{a}\bar{b}c d + \bar{a}b\bar{c}\bar{d} + \bar{a}b c \bar{d} + abcd \\
 = & \bar{a}\bar{b}\bar{d} + \bar{a}c\bar{d} + \bar{a}\bar{b}c\bar{d} + \bar{a}\bar{b}c d + \bar{a}b\bar{c}\bar{d} + \bar{a}b c \bar{d} + abcd \\
 = & \bar{a}\bar{d}(\bar{b} + c + b\bar{c}) + \bar{a}\bar{b}c\bar{d} + \bar{a}\bar{b}c d + \bar{a}b c \bar{d} + abcd \\
 = & \bar{a}\bar{b}\{(\bar{b} + c + b)(\bar{b} + c + \bar{c})\} + \bar{a}\bar{b}c\bar{d} + \bar{a}\bar{b}c d + \bar{a}b c \bar{d} + abcd \\
 = & \bar{a}\bar{d} + \bar{a}\bar{b}c\bar{d} + \bar{a}\bar{b}c d + \bar{a}b(c + \bar{d}) \\
 = & \bar{a}\bar{d} + \bar{a}\bar{b}c\bar{d} + \bar{a}\bar{b}c d + abc \\
 = & \bar{a}\bar{d} + \bar{a}\bar{b}c\bar{d} + ac(\bar{b} + b\bar{d}) \\
 = & \bar{a}\bar{d} + \bar{a}\bar{b}c\bar{d} + ac\bar{d} + abc \\
 = & \bar{d}(\bar{a} + ac) + \bar{a}\bar{b}c\bar{d} + abc \\
 = & \bar{d}(\bar{a} + c) + \bar{a}\bar{b}c\bar{d} + abc \\
 = & \bar{a}\bar{d} + c\bar{d} + \bar{a}\bar{b}c\bar{d} + abc \\
 = & \bar{a}\bar{b}\bar{a}\bar{d} + c(\bar{d} + \bar{a}\bar{b}\bar{d} + ab) \\
 = & \bar{a}\bar{d} + c[\{(\bar{d} + \bar{a}\bar{b}) \cdot (d + \bar{d})\} + ab] \\
 = & \bar{a}\bar{d} + c\bar{d} + \bar{a}\bar{b}c + abc
 \end{aligned}$$

#### 4. Experimental Result Analysis:

##### i. Circuit:

4.2.1: Verifying the result of the simplified version of the F in 4.1

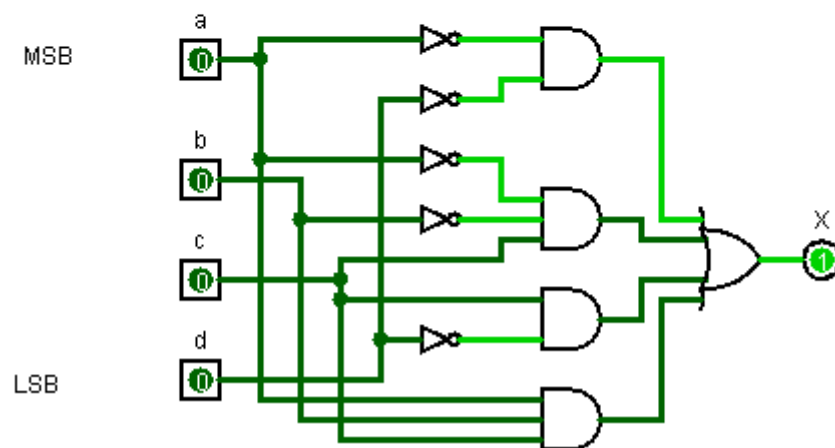


Figure: Circuit Diagram of the simplified version of F in 4.1

##### ii. Truth Table:

| a | b | c | d | X |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

**5. Conclusion:**

From the above experiment, we can conclude that the simplified version of the function  $F$  in 4.1 gives the same output as the original function. So the simplified version is verified.